

Basic Hardware Module Designs

Alex Yang

Engineering School, NPU

1. Encoder/Decoder

a) Encoder:

```
0000_0000_0000_0000 => 0000
0000_0000_0000_0001 => 0000
0000_0000_0000_0010 => 0001
0000_0000_0000_0100 => 0010
0000_0000_0000_1000 => 0011
... ...
1000_0000_0000_0000 => 1111
```

```
`define kDInBitW 16
`define kDInBitS `kDInBitW-1:0
`define kDOutBitW 4
`define kDOutBitS `kDOutBitW-1:0

module enc(
    dataIn_i,
    en_i,
    dataOut_o
);
    input[`kDInBitS] dataIn_i;
    input en_i;
    output[`kDOutBitS] dataOut_o;

    reg[`kDOutBitS] dataOut_o;

    always@(*)begin
        if(!en_i) dataOut_o= 4'b0000;
        else begin
            case(dataIn_i)
                16'h0002: dataOut_o=4'b0001;
                16'h0004: dataOut_o=4'b0010;
                16'h0008: dataOut_o=4'b0011;
                16'h0010: dataOut_o=4'b0100;
                16'h0020: dataOut_o=4'b0101;
                16'h0040: dataOut_o=4'b0110;
                16'h0080: dataOut_o=4'b0111;
                16'h0100: dataOut_o=4'b1000;
                16'h0200: dataOut_o=4'b1001;
                16'h0400: dataOut_o=4'b1010;
                16'h0800: dataOut_o=4'b1011;
                16'h1000: dataOut_o=4'b1100;
                16'h2000: dataOut_o=4'b1101;
                16'h4000: dataOut_o=4'b1110;
                16'h8000: dataOut_o=4'b1111;
                default: dataOut_o=4'bZZZZ;
            endcase
        end
    end
```

```

        endcase
    end
end
endmodule

```

b) Decoder;

```

0000 => 0000_0000_0000_0001
0001 => 0000_0000_0000_0010
0010 => 0000_0000_0000_0100
0011 => 0000_0000_0000_1000
0100 => 0000_0000_0001_0000
... ..
1111 => 1000_0000_0000_0000

```

```

`define kDInBitW 4
`define kDInBitS `kDInBitW-1:0
`define kDOutBitW 16
`define kDOutBitS `kDOutBitW-1:0

module dec(
    dataIn_i,
    en_i,
    dataOut_o
);
    input[`kDInBitS] dataIn_i;
    input en_i;
    output[`kDOutBitS] dataOut_o;

    reg[`kDOutBitS] dataOut_o;

    always@(*)begin
        if(!en_i) dataOut_o= 0;
        else begin
            case(dataIn_i)
                4'b0000: dataOut_o=`kDOutBitW'h0001;
                4'b0001: dataOut_o=`kDOutBitW'h0002;
                4'b0010: dataOut_o=`kDOutBitW'h0004;
                4'b0011: dataOut_o=`kDOutBitW'h0008;
                4'b0100: dataOut_o=`kDOutBitW'h0010;
                4'b0101: dataOut_o=`kDOutBitW'h0020;
                4'b0110: dataOut_o=`kDOutBitW'h0040;
                4'b0111: dataOut_o=`kDOutBitW'h0080;
                4'b1000: dataOut_o=`kDOutBitW'h0100;
                4'b1001: dataOut_o=`kDOutBitW'h0200;
                4'b1010: dataOut_o=`kDOutBitW'h0400;
                4'b1011: dataOut_o=`kDOutBitW'h0800;
                4'b1100: dataOut_o=`kDOutBitW'h1000;
                4'b1101: dataOut_o=`kDOutBitW'h2000;
                4'b1110: dataOut_o=`kDOutBitW'h4000;
                4'b1111: dataOut_o=`kDOutBitW'h8000;
                default: dataOut_o=`kDOutBitW'hZZZZ;
            endcase
        end
    end
endmodule

```

```

        end
    end
endmodule

```

2. Mux/Demux

a) Mux: 4-to-1

```

module mux4to1(
    a_i,
    b_i,
    c_i,
    d_i,
    sel_i,
    dOut_o
);
    input    a_i;
    input    b_i;
    input    c_i;
    input    d_i;
    input[1:0] sel_i;
    output    dOut_o;

    assign    dOut_o  =  (sel_i == 0)? a_i:
                        (sel_i == 1)? b_i:
                        (sel_i == 2)? c_i:
                        (sel_i == 3)? d_i: 1'bz;
end

```

b) Demux: 1-to-4

```

module demux4to1(
    dIn_i,
    sel_i,
    dOut_0
);
    input    dIn_i;
    input[1:0] sel_i;
    output[3:0] dOut_0;

    reg[3:0] dOut_0;

    always@(*)begin
        case(sel_i)
            2'b00: dOut_0[0] = dIn_i;
            2'b01: dOut_0[1] = dIn_i;
            2'b10: dOut_0[2] = dIn_i;
            2'b11: dOut_0[3] = dIn_i;
            default: dOut_0  = 4'bZZZZ;
        endcase
    end
endmodule

```

3. Counter

a) up-down counter with load

```
`define kBitW      8
`define kBitS      `kBitW-1:0
module counter(
    clk,
    rst,
    en_i,
    load_i,          // Enable starting counting value
    dataload_i,
    upDown_i,        // upDown_i = 0, count up
    dataOut_o
);
    input          clk;
    input          rst;
    input          en_i;
    input          load_i;
    input          upDown_i;
    input[`kBitS]  dataload_i;
    output[`kBitS] dataOut_o;

    reg[`kBitS]    dataOut_o;

    always@(posedge clk)begin
        if(rst)                dataOut_o <= 0;
        else if(en_i)begin
            if(load_i)          dataOut_o <= dataload_i;
            else if(upDown_i)   dataOut_o <= dataOut_o + 1;
                                dataOut_o <= dataOut_o - 1;
            else
                dataOut_o <= 0;
        end
    end
endmodule
```

b) Different base up-down counter with load

```
`define kBitW      4
`define kBitS      `kBitW-1:0
`define kBase      13

module counter(
    clk,
    rst,
    en_i,
    load_i,          // Enable starting counting value
    dataload_i,
    upDown_i,        // upDown_i = 1, count up
    dataOut_o
);
    input          clk;
```

```

input          rst;
input          en_i;
input          load_i;
input          upDown_i;
input[`kBitS] dataload_i;
output[`kBitS] dataOut_o;

reg[`kBitS]    dataOut_o;

always@(posedge clk)begin
    if(rst)    dataOut_o <= 0;
    else if(en_i)begin
        if(dataOut_o == (`kBase-1))    dataOut_o <= 0;
        else begin
            if(load_i)    dataOut_o <= dataload_i;
            else if(upDown_i)    dataOut_o <= dataOut_o + 1;
            else    dataOut_o <= dataOut_o - 1;
        end
    end
    else    dataOut_o <= 0;
end
endmodule


```

c) Linear Feedback Shift Register(LFSR)

i. Pseudo Random Number Generator

Bits	Feedback polynomial	Period
n		$2^n - 1$
2	$x^2 + x + 1$	3
3	$x^3 + x^2 + 1$	7
4	$x^4 + x^3 + 1$	15
5	$x^5 + x^3 + 1$	31
6	$x^6 + x^5 + 1$	63
7	$x^7 + x^6 + 1$	127
8	$x^8 + x^6 + x^5 + x^4 + 1$	255
9	$x^9 + x^5 + 1$	511
10	$x^{10} + x^7 + 1$	1023
11	$x^{11} + x^9 + 1$	2047
12	$x^{12} + x^{11} + x^{10} + x^4 + 1$	4095
13	$x^{13} + x^{12} + x^{11} + x^8 + 1$	8191

14	$x^{14} + x^{13} + x^{12} + x^2 + 1$	16383
15	$x^{15} + x^{14} + 1$	32767
16	$x^{16} + x^{14} + x^{13} + x^{11} + 1$	65535
17	$x^{17} + x^{14} + 1$	131071
18	$x^{18} + x^{11} + 1$	262143
19	$x^{19} + x^{18} + x^{17} + x^{14} + 1$	524287

 

Note: XNOR could allow seed=0 (initial values), seed≠1;
XOR allows seed=1 (initial values), seed≠0

```

`define kBitW      4
`define kBitS      `kBitW-1:0
module lfsrCnt(
    clk,
    rst,
    en_i,
    cnt_o,
    bitStr_o        //Overflow bit
);
    input          clk, rst;
    input          en_i;
    output[`kBitS] cnt_o;

    reg[`kBitS]    cnt_o;


    assign         bitStr_o = cnt_o[0];

    always@(posedge clk)begin
        if(rst)    cnt_o <= 0;
        else if(en_i) begin
            cnt_o[0] <= cnt_o[1] ;
            cnt_o[1] <= cnt_o[2];
            cnt_o[2] <= cnt_o[3];
            cnt_o[3] <= cnt_o[0] ^ cnt_o[1];
        end
    end
endmodule

```

- ii. Reverse random number generation by inverse LFSR
 - 1) change shift direction from right to left

 2) $x^1 - x^2 - x^3 - x^4$ rotate to the right as below



```

`define kBitW      4
`define kBitS      `kBitW-1:0
module lfsrCnt(
    clk,
    rst,
    en_i,
    cnt_o,
    bitStr_o        //Overflow bit
);
    input          clk, rst;
    input          en_i;
    output[`kBitS] cnt_o;

    reg[`kBitS]    cnt_o;

    assign         bitStr_o = cnt_o[3];

    always@(posedge clk)begin
        if(rst)    cnt_o <= 0;
        else if(en_i) begin
            cnt_o[0] <= cnt_o[3] ^ cnt_o[0];
            cnt_o[1] <= cnt_o[0];
            cnt_o[2] <= cnt_o[1];
            cnt_o[3] <= cnt_o[2] ;
        end
    end
endmodule

```

iii. up-down LFSR counter

```

`define kBitW      4
`define kBitS      `kBitW-1:0

module upDownLFSR(
    clk,
    rst,
    en_i,
    upDown_i,        //upDown_i = 1 -> up; othrwise down
    cnt_o,
    bitStr_o        //Overflow bit
);
    input          clk;
    input          rst;
    input          en_i;
    input          upDown_i;

```

```

output[`kBitS]      cnt_o;

reg[`kBitS]         cnt_o;

assign      bitStr_o = (len_i)?      1'b0      :
                      (upDown_i)?    cnt_o[0] : cnt_o[3] ;

always@(posedge clk)begin
    if(rst)      cnt_o <= 0;
    else if(en_i)begin
        if(upDown_i)begin
            cnt_o[0] <= cnt_o[1] ;
            cnt_o[1] <= cnt_o[2];
            cnt_o[2] <= cnt_o[3];
            cnt_o[3] <= cnt_o[0] ^ cnt_o[1];
        end
        else begin
            cnt_o[0] <= cnt_o[3] ^ cnt_o[0];
            cnt_o[1] <= cnt_o[0];
            cnt_o[2] <= cnt_o[1];
            cnt_o[3] <= cnt_o[2] ;
        end
    end
    else      cnt_o <= 0;
end
endmodule


```

4. Frequency Divider (Don't use in RTL design)

Case1: divided by integer number A, such as 5

Step1: rising/falling edge counter: 0~4 ($A-1 = 5-1$)

 Step2: observe 0~2 (a little bit bigger than $5/2$ cycles) and compare two waveforms as follows




$$\text{outClk} = (\text{rEdgeCnt} < 3 \ \&\& \ \text{fEdgeCnt} < 3) ? 1'b1 : 1'b0$$

Case2: divided by x.5, such as 4.5 and hi-voltage duty 2.5 cycles /low 2 cycles

Step1: rising/falling edge counter: 0~8 ($8 = 4.5 \times 2 - 1$)

 Step2: observe 0.5~2 in rEdgeCnt for hi-voltage duty and low in cycle 3~4 and cycle 7~8 in fEdgeCnt, and then compare two waveforms as follows



$$\text{outClk} = ((\text{rEdgeCnt} > 2 \ \&\& \ \text{rEdgeCnt} < 5) \parallel \text{fEdgeCnt} > 6) ? 1'b0 : 1'b1$$

a) Divided by 3

```
module Div3(
    clk,
    rst,
    clkOut_o
);
    input    clk;
    input    rst;
    output   clkOut_o;

    reg[1:0] rEdgeCnt_r;
    reg[1:0] fEdgeCnt_r;

    assign    clkOut_o = ((rEdgeCnt_r != 2) && (fEdgeCnt_r != 2));

    always@(posedge clk)begin
        if(rst)            rEdgeCnt_r <= 0;
        else if(rEdgeCnt_r == 2) rEdgeCnt_r <= 0;
        else                rEdgeCnt_r <= rEdgeCnt_r + 1;
    end

    always@(negedge clk)begin
        if(rst)            fEdgeCnt_r <= 0;
        else if(fEdgeCnt_r == 2) fEdgeCnt_r <= 0;
        else                fEdgeCnt_r <= fEdgeCnt_r + 1;
    end
end
endmodule
```

b) Divided by 5

```
module Div5(
    clk,
    rst,
    clkOut_o
);
    input    clk;
    input    rst;
    output   clkOut_o;

    reg[2:0] rEdgeCnt_r;
```

```

reg[2:0]      fEdgeCnt_r;

assign        outClk = (rEdgeCnt <3 && fEdgeCnt < 3)? 1'b1: 1'b0;

always@(posedge clk)begin
    if(rst)                rEdgeCnt_r <= 0;
    else if(rEdgeCnt_r == 4)rEdgeCnt_r <= 0;
    else                    rEdgeCnt_r <= rEdgeCnt_r + 1;
end

always@(negedge clk)begin
    if(rst)                fEdgeCnt_r <= 0;
    else if(fEdgeCnt_r == 4)fEdgeCnt_r <= 0;
    else                    fEdgeCnt_r <= fEdgeCnt_r+ 1;
end
endmodule

```

c) Divided by 4.5

```

module Div45(
    clk,
    rst,
    clkOut_o
);
    input    clk;
    input    rst;
    output    clkOut_o;

    reg[3:0]  rEdgeCnt_r;
    reg[3:0]  fEdgeCnt_r;

    assign    outClk = ((rEdgeCnt >2 && rEdgeCnt < 5) || fEdgeCnt >6 ) ? 1'b0: 1'b1

    always@(posedge clk)begin
        if(rst)                rEdgeCnt_r <= 0;
        else if(rEdgeCnt_r == 8)rEdgeCnt_r <= 0;
        else                    rEdgeCnt_r <= rEdgeCnt_r + 1;
    end

    always@(negedge clk)begin
        if(rst)                fEdgeCnt_r <= 0;
        else if(fEdgeCnt_r == 8)fEdgeCnt_r <= 0;
        else                    fEdgeCnt_r <= fEdgeCnt_r+ 1;
    end
endmodule

```

5. Edge Detectors

a) Rising edge detector

```

module      risingDet(
    clk,
    rst,
    dIn_i,          //Synchronized data in
    risingPulse_o
);

```

```

input      clk;
input      rst;
input      dIn_i;
output     risingPulse_o;

reg        oneDelayDin_r;

assign     risingPulse_o = dIn_i & ~oneDelayDin_r;

always@(posedge clk)begin
    if(rst)    oneDelayDin_r <= 0;
    else      oneDelayDin_r <= dIn_i;
end

endmodule

```

b) Falling edge detector

```

module     fallingDet(
            clk,
            rst,
            dIn_i,
            fallingPulse_o
);
    input    clk;
    input    rst;
    input    dIn_i;
    output   fallingPulse_o;

    reg      oneDelayDin_r;

    assign   fallingPulse_o = ~dIn_i & oneDelayDin_r;

    always@(posedge clk)begin
        if(rst)    oneDelayDin_r <= 0;
        else      oneDelayDin_r <= dIn_i;
    end
endmodule

```

c) Raising/Falling edge detectors

```

module     edgeDet(
            clk,
            rst,
            dataIn_i,
            risingPulse_o,
            fallingPulse_o
);
    input    clk;
    input    rst;
    input    dIn_i;
    output   risingPulse_o;
    output   fallingPulse_o;

    reg      oneDelayDin_r;

```

```

assign      risingPulse_o = dIn_i & ~oneDelayDin_r;
assign      fallingPulse_o = ~dIn_i & oneDelayDin_r;

always@(posedge clk)begin
    if(rst)    oneDelayDin_r <= 0;
    else      oneDelayDin_r <= dIn_i;
end
endmodule

```

6. Memory Design (Only for simulation, **non-synthesizable**)

a) Single port

```

module syncRAM (
    clk,          // Clock Input
    address,      // Address Input
    data,         // Data bi-directional
    cs,          // Chip Select
    we,          // Write Enable/Read Enable
    oe           // Output Enable
);

parameter pBitW = 8;
parameter pAdrW = 8;
parameter pRAMDep = 1 << pAdrW;

input          clk;
input [pAdrW-1:0] address;
input          cs;
input          we;
input          oe;

inout [pBitW-1:0] data;

reg [pBitW-1:0] dOut_r;
reg [pBitW-1:0] mem [0:pRAMDep-1];
reg            oe_r;

// Tri-State Buffer control
// output : When we = 0, oe = 1, cs = 1
assign      data = (cs && oe && !we) ? dOut_r : 8'bz;

// Memory Write Block
// Write Operation : When we = 1, cs = 1
always @ (posedge clk)begin
    if ( cs && we ) begin
        mem[address] = data;
    end
end

// Memory Read Block
// Read Operation : When we = 0, oe = 1, cs = 1
always @ (posedge clk)begin

```

```

        if (cs && !we && oe) begin
            dOut_r = mem[address];
            oe_r = 1;
        end else begin
            oe_r = 0;
        end
    end
end
endmodule

module asyncRAM (
    clk,
    address,      // Address Input
    data,         // Data bi-directional
    cs,           // Chip Select
    we,           // Write Enable/Read Enable
    oe            // Output Enable
);

    parameter pBitW = 8;
    parameter pAdrW = 8 ;
    parameter pRAMDep = 1 << pAdrW;

    input          clk;
    input [pAdrW-1:0] address;
    input          cs;
    input          we;
    input          oe;

    inout [pBitW-1:0] data;

    reg [pBitW-1:0] dOut_r;
    reg [pBitW-1:0] mem [0 : pRAMDep-1];

    // Tri-State Buffer control
    // output : When we = 0, oe = 1, cs = 1
    assign      data = (cs && oe && !we) ? dOut_r : 8'bz;

    // Memory Write Block
    // Write Operation : When we = 1, cs = 1
    always @ (posedge clk)begin
        if ( cs && we ) begin
            mem[address] = data;
        end
    end

    // Memory Read Block
    // Read Operation : When we = 0, oe = 1, cs = 1
    always @ (address or cs or we or oe)begin
        if (cs && !we && oe) begin
            dOut_r = mem[address];
        end
    end
end
endmodule

```

b) Dual port

```

module dualSyncRAM(
    clk,           // Clock Input
    address0,      // address0 Input
    data0,         // data0 bi-directional
    cs0,           // Chip Select
    we0,           // Write Enable/Read Enable
    oe0,           // Output Enable
    address1,      // address1 Input
    data1,         // data1 bi-directional
    cs1,           // Chip Select
    we1,           // Write Enable/Read Enable
    oe1            // Output Enable
);

parameter pDataW = 8 ;
parameter pAdrW  = 8 ;
parameter pRAMDep = 1 << pAdrW;

input [pAdrW-1:0]    address0 ;
input               cs0 ;
input               we0 ;
input               oe0 ;
input [pAdrW-1:0]    address1 ;
input               cs1 ;
input               we1 ;
input               oe1 ;

inout [pDataW -1:0]  data0 ;
inout [pDataW -1:0]  data1 ;

reg [pDataW -1:0]    dOut0_r ;
reg [pDataW -1:0]    dOut1_r ;
reg [pDataW -1:0]    mem [0 : pRAMDep-1];

// Memory Write Block
// Write Operation : When we0 = 1, cs0 = 1
always @ (posedge clk)begin
    if ( cs0 && we0 ) begin
        mem[address0] <= data0;
    end else if (cs1 && we1) begin
        mem[address1] <= data1;
    end
end

// Tri-State Buffer control
// output : When we0 = 0, oe0 = 1, cs0 = 1
assign    data0 = (cs0 && oe0 && !we0) ? dOut0_r : 8'bzz;

// Memory Read Block
// Read Operation : When we0 = 0, oe0 = 1, cs0 = 1
always @ (posedge clk)begin

```

```

        if (cs0 && !we0 && oe0) begin
            dOut0_r <= mem[address0];
        end else begin
            dOut0_r <= 0;
        end
    end

    //Second Port of RAM
    // Tri-State Buffer control
    // output : When we0 = 0, oe0 = 1, cs0 = 1

    assign data1 = (cs1 && oe1 && !we1) ? dOut1_r : 8'bz;

    // Memory Read Block 1
    // Read Operation : When we1 = 0, oe1 = 1, cs1 = 1
    always @ (posedge clk)begin
        if (cs1 && !we1 && oe1) begin
            dOut1_r <= mem[address1];
        end else begin
            dOut1_r <= 0;
        end
    end
endmodule

module dualAsyncRAM (
    address0,           // address0 Input
    data0,              // data0 bi-directional
    cs0,               // Chip Select
    we0,               // Write Enable/Read Enable
    oe0,               // Output Enable
    address1,          // address1 Input
    data1,              // data1 bi-directional
    cs1,               // Chip Select
    we1,               // Write Enable/Read Enable
    oe1,               // Output Enable
);

    parameter pDataW = 8 ;
    parameter pAdrW = 8 ;
    parameter pRAMDep = 1 << pAdrW;

    input [pDataW-1:0]    address0 ;
    input                cs0 ;
    input                we0 ;
    input                oe0 ;
    input [pDataW-1:0]    address1 ;
    input                cs1 ;
    input                we1 ;
    input                oe1 ;

    inout [pDataW-1:0]    data0 ;
    inout [pDataW-1:0]    data1 ;

```

```

reg [pDataW-1:0]      dOut0_r ;
reg [pDataW-1:0]      dOut1_r ;
reg [pDataW-1:0]      mem [0 : pRAMDep-1];

// Memory Write Block
// Write Operation : When we0 = 1, cs0 = 1
always @ (address0 or cs0 or we0 or data0 or address1 or cs1 or we1 or data1)begin
    if ( cs0 && we0 ) begin
        mem[address0] <= data0;
    end else if (cs1 && we1) begin
        mem[address1] <= data1;
    end
end

// Tri-State Buffer control
// output : When we0 = 0, oe0 = 1, cs0 = 1

assign data0 = (cs0 && oe0 && !we0) ? dOut0_r : 8'bz;

// Memory Read Block
// Read Operation : When we0 = 0, oe0 = 1, cs0 = 1
always @ (address0 or cs0 or we1 or oe0)begin
    if (cs0 && !we0 && oe0) begin
        dOut0_r <= mem[address0];
    end else begin
        dOut0_r <= 0;
    end
end

//Second Port of RAM
// Tri-State Buffer control
// output : When we0 = 0, oe0 = 1, cs0 = 1

assign data1 = (cs1 && oe1 && !we1) ? dOut1_r : 8'bz;

// Memory Read Block 1
// Read Operation : When we1 = 0, oe1 = 1, cs1 = 1
always @ (address1 or cs1 or we1 or oe1)begin
    if (cs1 && !we1 && oe1) begin
        dOut1_r <= mem[address1];
    end else begin
        dOut1_r <= 0;
    end
end

end
endmodule

```

7. Parity & CRC

a) Parity

- i Even parity bit = 0 if # of 1's in input data is even; Even parity bit = 1 if # of 1's is odd.
- ii Odd parity bit = 0 if # of 1's is odd; Even parity bit = 1 if # of 1's is even.

iii Even/Odd Parity Bit Generation Verilog Code:

```

`define      kBitW      8
`define      kBitS      `kBitW-1:0

module  parityBitGen(
                                dataIn_i,
                                dataOut_o
);
    input[`kBitW-2:0]  dataIn_i;
    output[`kBitS]     dataOut_o;

    assign              dataOut_o = (^dataIn_i)? {1, dataIn_i} : {0, dataIn_i}; //Even parity
    //assign            dataOut_o = (^dataIn_i)? {0, dataIn_i} : {1, dataIn_i}; //Odd parity

endmodule

```

b) CRC (cyclic redundancy check)


i. Serial CRC encoder:

e.g. dataIn = 1010
 If $g(x) = x^3 + x + 1$, dataOut(with CRC) = 1010 xxx;
 $x^3 + x + 1 \Rightarrow b3b2b1b0 = 1011$
 $xxx(dataCRC) = 1010\ 000 \% 1011 = 011$
 dataOut = 1010 011

Hardware implementation:

dataIn = {1, 0, 1, 0}, after 4 clock cycles, dataCRC = 011;

 $g(x) = x^3 + x + 1 \Rightarrow$ in shift register, x^3 (b2) is output and then xor dataIn to x ; x (b0) is output and then xor (dataIn xor x^3) to $b1$ (x^2);



e.g. $g(x) = x^4 + x^2 + x + 1 \Rightarrow$ in DFF, x^4 (b3) is output and then xor dataIn to x ; x (b0) is output and then xor (dataIn xor x^4) to x^2 ; x^2 (b1) is output and then xor (dataIn xor x^4) to x^3 ;

GENERATOR POLYNOMIALS OF SOME CRC CODES

Common Name	r	Generator	
		Polynomial	Hex
CRC-12	12	$x^{12} + x^{11} + x^3 + x^2 + x + 1$	80F
CRC-16	16	$x^{16} + x^{15} + x^2 + 1$	8005
CRC-CCITT	16	$x^{16} + x^{12} + x^5 + 1$	1021
CRC-32	32	$x^{32} + x^{26} + x^{23} + x^{22} + x^{16} + x^{12} + x^{11} + x^{10} + x^8 + x^7 + x^5 + x^4 + x^2 + x + 1$	04C11DB7

Note: CCITT(International Telegraph and Telephone Consultative Committee)

Other CRC generation polynomials, for example, are as follows.

Common Name	r	Generation Polynomial
CRC-3	3	$x^3 + x + 1$
CRC-4	4	$x^4 + x^2 + x + 1$
CRC-5	5	$x^5 + x^2 + 1$
CRC-6	6	$x^6 + x + 1$
CRC-8	8	$x^8 + x^5 + x^4 + 1$

```

module serialCRC3(
    clk,
    rst,
    en_i,
    dIn_i,           // 4 bits
    dOut_o           // 3 bits CRC code
);
    input      clk;
    input      rst;
    input      en_i;
    input      dIn_i;
    output[2:0] dOut_o;

    reg[2:0]    lfsr_r;


    assign      dOut_o = lfsr_r;

    // Generation polynomial:  $x^3 + x + 1$ 
    always@(posedge clk)begin
        if(rst)        lfsr_r <= 3'b000;
        else if(en_i)begin
            lfsr_r[2] <= lfsr_r[1];
            lfsr_r[1] <= lfsr_r[0] ^ lfsr_r[2] ^ dIn_i;
            lfsr_r[0] <= lfsr_r[2] ^ dIn_i;
        end
    end
endmodule

```

 ii. Serial CRC decoder:

dataIn={ 1,0,1,0,0,1,1 } after 7 clock cycles, if remOut = 000, there are not any errors. If remOut is equal to zero, there is at least 1 error.



iii. Parallel CRC encoder

```
module crc5Parallel(
    input [3:0]          dataIn,
    output reg[4:0]      crc5,
    input               rst,
    input               clk
);
    // LFSR for USB CRC5  $g(x) = x^5 + x^2 + 1$ 
    function [4:0] crc5Serial;
        input [4:0]      crc;
        input             data;
        begin
            crc5Serial[0] = crc[4] ^ data;
            crc5Serial[1] = crc[0];
            crc5Serial[2] = crc[1] ^ crc[4] ^ data;
            crc5Serial[3] = crc[2];
            crc5Serial[4] = crc[3];
        end
    endfunction
    // 4 iterations of USB CRC5 LFSR
    function [4:0] crcIteration;
        input [4:0]      crc;
        input [3:0]      data;
        integer          i;
        begin
            crcIteration = crc;
            for(i=0; i<4; i=i+1)
                crcIteration = crc5Serial(crcIteration, data[3-i]);
            end
        endfunction
    always @(posedge clk) begin
        if(rst)      crc5 <= 5'h00;
        else         crc5 <= crcIteration(crc5,dataIn);
    end
endmodule
```

iv. Parallel CRC decoder

1. Hardware structure is the same as encoder, but number of input bits is different.