

# Northwestern Polytechnic University

## EE461 Digital Design and HDL

### Examples of Logic Synthesis Scripting

#### I. Examples of Combinational Logic Synthesis in RTL

##### 1. One-Bit Full Adder Design in Continuous Assignment

###### RTL Level Design (File Name: oneBitFA1.v):

```
module oneBitFA1(  
    input wire a_i,  
    input wire b_i,  
    input wire ci_i,  
    output wire sum_o,  
    output wire co_o  
);  
    assign {co_o,sum_o} = a_i + b_i + ci_i;  
endmodule
```

###### Logic Synthesis:


```
>> vi oneBitFA1Syn.scr  
include /ee/setup/synopsys/synopsys_setup_npu018.inc  
read -f verilog oneBitFA1.v  
current_design = oneBitFA1  
link  
compile  
create_schematic  
plot -output oneBitFA1.ps  
write -f verilog -o oneBitFA1.vs -hierarchy  
exit  
>> source /ee/setup/synopsys/setup.cmd  
>> dc_shell -f oneBitFA1Syn.scr  
>>ls
```

**Notes:** You will find two files oneBitFA1.vs and oneBitFA1.ps. oneBitFA1.vs is Verilog module in gate level (Netlist) after logic synthesis, but oneBitFA1.ps is a schematic of this synthesized netlist. Convert it to pdf file by


```
>> ps2pdf oneBitFA1.ps  
>>ls
```

Congratulations! You've got oneBitFA1.pdf file with 1-bit full adder schematic. If you want to move it to your windows system and open it. Please follow the instructions as follows.


- 1) Open "Xmanager", click "Xftp"

 


2) Select “File -> New”

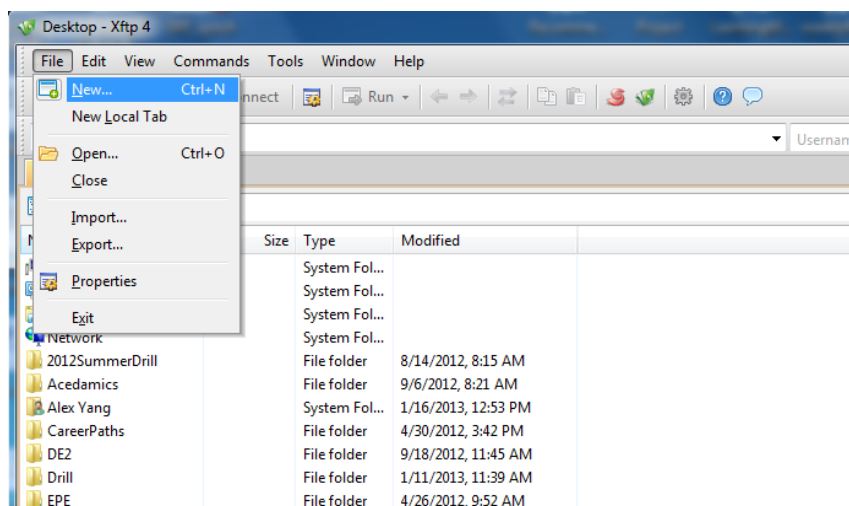

 
3) Fill in the form as below, and then click OK.




4) Click “Connect”

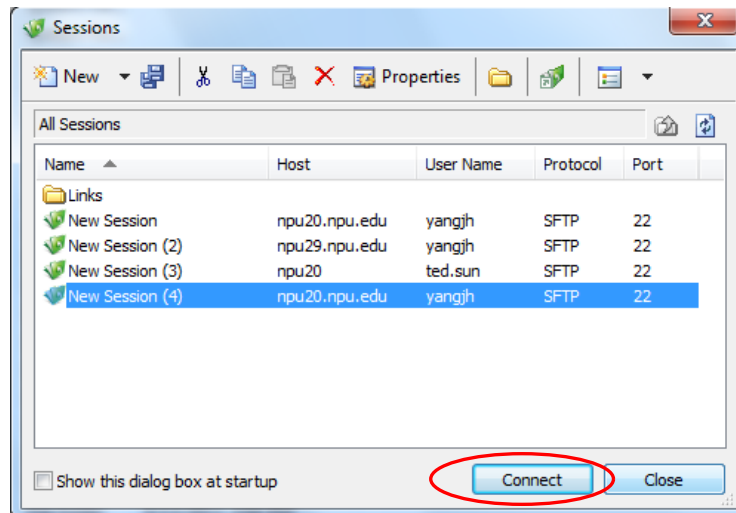

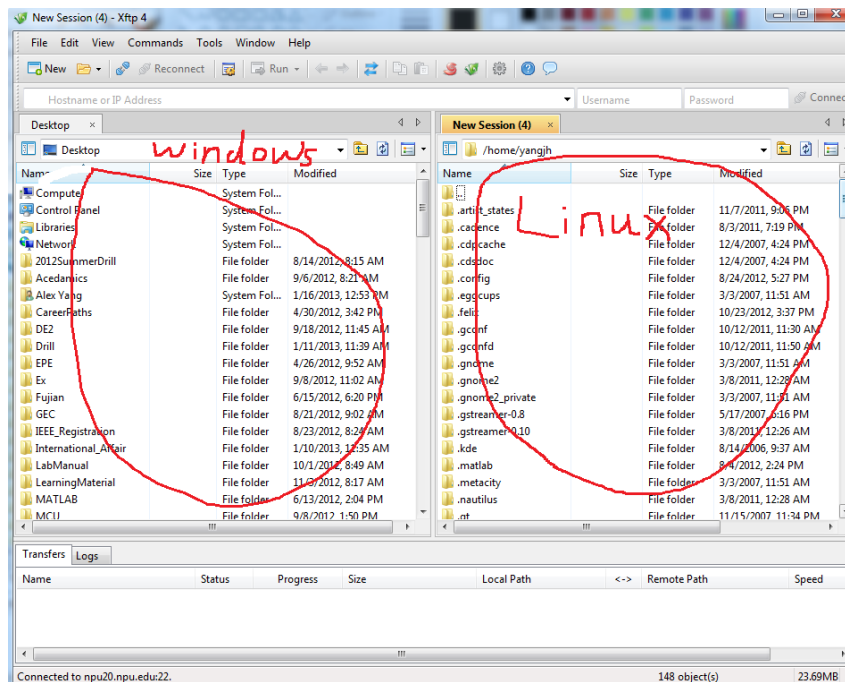5) Select the file that you want to move between two systems, and hold & drag from the window to the other.



 6) Check the schematic by opening pdf file.



## 2. One-Bit Full Adder Design in “always” block

### RTL Level Design (File Name: oneBitFA2.v):

```
module oneBitFA2(  
    input wire a_i,  
    input wire b_i,  
    input wire ci_i,  
    output reg sum_o,  
    output reg co_o  
);  
  
    always @(a_i, b_i, ci_i)begin  
        {co_o, sum_o} = a_i + b_i + ci_i;  
    end  
endmodule
```

### Logic Synthesis:

>> vi oneBitFA2Syn.scr

```
include /ee/setup/synopsys/synopsys_setup_npu018.inc  
read -f verilog oneBitFA2.v  
current_design = oneBitFA2  
link  
compile  
create_schematic  
plot -output oneBitFA2.ps  
write -f verilog -o oneBitFA2.vs -hierarchy  
exit
```

>> source /ee/setup/synopsys/setup.cmd

>> dc\_shell -f oneBitFA2Syn.scr

>>ls

Open schematic pdf file to compare with example as above.

## II. Examples of Sequential Logic Synthesis in RTL

### 1. Logic Synchronous DFF

#### RTL Level Design (File Name: DFFSynch.v):

```
module DFFSynch(  
    d_i,  
    rst_i,  
    clk,  
    q_o  
);  
  
    input d_i,rst_i,clk;  
    output q_o;  
  
    reg q_o;  
  
    always @(posedge clk)begin  
        if(rst_i) q_o <= 0;  
        else q_o <= d_i;  
    end  
endmodule
```

### 2. Logic Asynchronous DFF

#### RTL Level Design (File Name: DFFASynch.v):

```
module DFFASynch(  
    d_i,  
    rst_i,  
    clk,  
    q_o  
);  
  
    input d_i,rst_i,clk;  
    output q_o;
```

```
    reg q_o;

    always @(posedge clk or posedge rst_i)begin
        if(rst_i)    q_o <= 0;
        else        q_o <= d_i;
    end
endmodule
```