



EE461 Verilog-HDL

Week 10 Logic Synthesis



Alex Yang, Engineering School, NPU



Week 10 Outlines

- Logic Synthesis
 - Synthesis supported/non-supported verilog structures
 - Directives: full case/parallel case
 - Coding Guideline





Synthesis supported/non-supported

■ synthesis supported

Ports: input, output, inout
wire, reg, tri
parameter
continuous assignment
always
task(w/o timing info) & function
for loop, if-else(if-else if-else), case

■ synthesis non-supported

=== , !==
/ (division)
% (modulus)
real, time
arrays of integer
defparam
delay (like #10)
assign & deassign/ force & release
primitive
initial block
repeat, forever, while
wait
fork / join
event



full_case/parallel_case

- "full_case" Directive in Case Statement
 - "full" in case block without "//synopsys full_case"
 - "full" in case block with "//synopsys full_case"

```
module ex(y, a, b, c, sel);  
    output    y;  
    input [1:0] sel;  
    input     a, b, c;  
    reg y;  
  
    always @(a or b or c or sel)  
        case(sel) // synopsys full_case  
            2'b00: y = a;  
            2'b01: y = b;  
            2'b10: y = c;  
        endcase  
    endmodule
```

directive: // synopsys full_case

For verilog simulator: it is a comment

For logic synthesizer: it is to tell that all outputs(**y** in above code) are equal to **x** for non-covered case, such as sel=2'b11.



full_case/parallel_case

- "full_case" Directive in Case Statement
 - "not full" in case block w/o "//synopsys full_case"

```
module ex(y, a, b, c, sel);  
  output    y;  
  input [1:0] sel;  
  input     a, b, c;  
  reg y;  
  
  always @(a or b or c or sel)  
    case (sel)  
      2'b00: y = a;  
      2'b01: y = b;  
      2'b10: y = c;  
    endcase  
endmodule
```

No "// synopsys full_case" &w/o default:

It will be inferred a latch for sure.



full_case/parallel_case

- "full_case" Directive in Case Statement
 - "full" in case block w/o "//synopsys full_case"

```
module ex(y, a, b, c, sel);  
  output      y;  
  input [1:0] sel;  
  input      a, b, c;  
  reg y;  
  
  always @(a or b or c or sel)  
    case (sel)  
      2'b00: y = a;  
      2'b01: y = b;  
      2'b10: y = c;  
      //default: y = 1'bx;  
      default: y = 1'b0;  
    endcase  
endmodule
```

No "// synopsys full_case" with default:

No latch inferred for $y=1'bx$, but mismatch exists between synthesis(x in synthesis: don't care; minimization involved) and simulation(x in simulation: unknow; logic operation involved, such as $b=a\&\sim a \Rightarrow b=0$ but $a=1'bx \Rightarrow b=1'bx$).

Correction default statement: all outputs = const. or one of values in other case statement



full_case/parallel_case

- "full_case" Directive in Case Statement
 - "full" in case block w/o "//synopsys full_case"

```
module ex(y, a, b, c, sel);  
    output    y;  
    input [1:0] sel;  
    input     a, b, c;  
    reg y;  
  
    always @(a or b or c or sel)  
        y = 1'b0;  
        case (sel)  
            2'b00: y = a;  
            2'b01: y = b;  
            2'b10: y = c;  
        endcase  
    endmodule
```

no "// synopsys full_case" & no default:

No latch inferred in case statement with **output values assignment to const. or one of values in other case statements.**

It is perfect match between synthesis and simulation.



full_case/parallel_case

- "full_case" Directive in Case Statement
 - "not full" in case block w/ "//synopsys full_case"

```
module ex(y, a, b, c, sel);  
  output      y;  
  input [1:0] sel;  
  input      a, b, c;  
  reg y;  
  
  always @(a or b or c or sel)  
    case (sel) // synopsys full_case  
      2'b00: y = a;  
      2'b01: y = b;  
      2'b10: y = c;  
    endcase  
endmodule
```

"// synopsys full_case" & not full case

No latch inferred after synthesis (gate level module), but mismatch exists between synthesis and simulation(a latch inferred in RTL level module).



full_case/parallel_case

- "full_case" Directive in Case Statement
 - "full" in case block w/ "//synopsys full_case"

```
module addrDecode1a (  
    mce0_n,  
    mce1_n,  
    rce_n, addr);  
    output    mce0_n, mce1_n,  
    rce_n;  
    input [31:30]  addr;  
    reg          mce0_n, mce1_n,  
    rce_n;  
  
    always @(addr)begin  
        casez (addr) // synopsys full_case  
            2'b10: {mce1_n, mce0_n} = 2'b10;  
            2'b11: {mce1_n, mce0_n} = 2'b01;  
            2'b0?:          rce_n = 1'b0;  
        endcase  
    end  
endmodule
```

"// synopsys full_case" & full case


latch inferred after synthesis (gate level module), because **not all outputs are assigned values.**





full_case/parallel_case

 - "full_case" Directive in Case Statement
 - Myth (Wrong): "//synopsys full_case" could remove all latches.
 - Truth: The easiest way to eliminate latches is to make initial default value assignments to all outputs immediately beneath the sensitivity list, before executing the case statement.





full_case/parallel_case

■ "full_case" Directive in Case Statement

Correct coding style:

```
module addrDecode1d (mce0_n, mce1_n, rce_n, addr);
    output          mce0_n, mce1_n, rce_n;
    input [31:30]   addr;
    reg             mce0_n, mce1_n, rce_n;

    always @(addr) begin
        // Assign values to all outputs
        {mce1_n, mce0_n, rce_n} = 3'b111;
        casez (addr)
            2'b10: {mce1_n, mce0_n} = 2'b10;
            2'b11: {mce1_n, mce0_n} = 2'b01;
            2'b0?: rce_n = 1'b0;

        endcase
    end
endmodule
```



full_case/parallel_case

- "parallel_case" Directive
 - A "parallel" case statement is a case statement in which it is only possible to match a case expression to one and only one case item. If it is possible to find a case expression that would match more than one case item, the matching case items are called "overlapping" case items and the case statement is not "parallel."





full_case/parallel_case

- "parallel_case" Directive in Case
 - "non parallel" in case block w/o "//synopsys parallel_case"

```
module intctl1a (int2, int1, int0, irq);  
  output int2, int1, int0;  
  input [2:0] irq;  
  reg int2, int1, int0;  
  always @(irq) begin  
    { int2, int1, int0 } = 3'b0;  
    casez (irq)  
      3'b1??: int2 = 1'b1;  
      3'b?1?: int1 = 1'b1;  
      3'b??1: int0 = 1'b1;  
    endcase  
  end  
endmodule
```

No "// synopsys parallel_case":

Simulation: a priority encoder

Synthesis: inferred a priority encoder



full_case/parallel_case

- "parallel_case" Directive in Case
 - "non parallel" in case block w/ "//synopsys parallel_case"

```
module intctl1a (int2, int1, int0, irq);  
  output int2, int1, int0;  
  input [2:0] irq;  
  reg int2, int1, int0;  
  always @(irq) begin  
    { int2, int1, int0} = 3'b0;  
    casez (irq) // synopsys parallel_case  
      3'b1??: int2 = 1'b1;  
      3'b?1?: int1 = 1'b1;  
      3'b???1: int0 = 1'b1;  
    endcase  
  end  
endmodule
```

w/ "// synopsys parallel_case":

Simulation: a priority encoder

Synthesis: non-priority encoder

mismatch between both



full_case/parallel_case

- "parallel_case" Directive in Case
 - "parallel" in case block w/o "//synopsys parallel_case"

```
module intctl1a (int2, int1, int0, irq);  
  output int2, int1, int0;  
  input [2:0] irq;  
  reg int2, int1, int0;  
  always @(irq) begin  
    { int2, int1, int0} = 3'b0;  
    casez (irq)  
      3'b1??: int2 = 1'b1;  
      3'b01?: int1 = 1'b1;  
      3'b001: int0 = 1'b1;  
    endcase  
  end  
endmodule
```

w/o "// synopsys
parallel_case":

Simulation: non-priority
encoder

Synthesis: a priority encoder

mismatch between both



full_case/parallel_case

- "parallel_case" Directive in Case
 - "parallel" in case block w/ "//synopsys parallel_case"

```
module intctl1a (int2, int1, int0, irq);  
  output int2, int1, int0;  
  input [2:0] irq;  
  reg int2, int1, int0;  
  always @(irq) begin  
    { int2, int1, int0} = 3'b0;  
    casez (irq) // synopsys parallel_case  
      3'b1??: int2 = 1'b1;  
      3'b01?: int1 = 1'b1;  
      3'b001: int0 = 1'b1;  
    endcase  
  end  
endmodule
```

w/ "// synopsys parallel_case":

Simulation: non-priority
encoder

Synthesis: a priority encoder

mismatch between both

Redundancy: "synopsys
parallel_case"



full_case/parallel_case

- Summary
 - Conclusion: "full_case" and "parallel_case" directives are most dangerous when they work! It is better to code a full and parallel case statement than it is to use directives to make up for poor coding practices.





full_case/parallel_case

■ Coding Style Guidelines

- Exercise caution when using the Verilog casez statement in RTL design
- Do not use casex in RTL design
- In general, do not use "full_case parallel_case" directives
- There are exceptions, but you have to know what you're doing if you plan to add "full_case parallel_case" directives.
- Coding with case statements is recommended when a truth-table-like structure makes the Verilog code more concise and readable.
- only use full_case parallel_case to optimize onehot FSM designs.
- When coding a case statement with "don't cares," use a casez statement and use "?" characters instead of "z" characters in the case items to indicate "don't care" bits.



Coding Guidelines

- Look at word file

