

Synchronization

Alex Yang

Engineering School, NPU

1. Single bit synchronizer

a) $T_{\text{asyncIn}} > T_{\text{clock}}$

```
module sync(
    clk,
    rst,
    asyncIn_i,
    syncOut_o
);
    input    clk;
    input    rst;
    input    asyncIn_i;
    output   syncOut_o;

    reg      syncOut_o;
    reg      oneDelayIn_r;

    always@(posedge clk or negedge rst)begin //Async. DFF
        if(!rst)begin
            oneDelayIn_r <= 0;
            syncOut_o <= 0;
        else {syncOut_o, oneDelayIn_r } <= {oneDelayIn_r, asyncIn_i};
        end
    end
endmodule
```

b) $T_{\text{asyncIn}} < T_{\text{clock}}$

```
module sync(
    clk,
    rst,
    asyncIn_i,
    syncOut_o
);
    input    clk;
    input    rst;
    input    asyncIn_i;
    output   syncOut_o;

    reg      syncOut_o;
    reg      StageOneOut_r;
    reg      StageTwoOut_r;

    wire     StageOneRst;
```

```

assign      firstStageRst = syncOut_o && ~asyncIn_i;

always@(posedge asyncIn_i or negedge firstStageRst )begin
    if(!firstStageRst)    StageOneOut_r <= 0;
    else                  StageOneOut_r <= 1;
end

always@(posedge clk or posedge rst)begin    //Async. DFF
    if(!rst)begin
        StageTwoOut_r <= 0;
        syncOut_o <= 0;
    else    {syncOut_o, StageTwoOut_r} <= {StageTwoOut_r, StageOneOut_r};

end
endmodule

```

2. More bits handshaking protocol(4-phase rule)

```

`define    kDataW            8
`define    kDataB            `kDataW-1:0

module handShakeSender(
    clk1_i,
    rst1_i,
    dataIn_i,
    sendReady_i,
    ack_i,
    req_o,
    dataOut_o
);

    input          clk1_i;
    input          rst1_i;
    input[ `kDataB] dataIn_i;
    input          sendReady_i;
    input          ack_i;
    output         req_o;
    output[ `kDataB] dataOut_o;

    reg[ `kDataB]    dataOut_o;
    reg              req_o;

    reg              ack_r;
    reg              synAck_r;

    reg              curSt_r;
    reg              nxtSt_r;

```

```

parameter          pStart = 1'b0;
parameter          pWait = 1'b1;

//Sending synchronized data from input data
always@(posedge clk1_i)begin
    if(rst1_i)                dataOut_o <= 0;
    else if(sendReady_i)      dataOut_o <= dataIn_i;
    else                      dataOut_o <= dataOut_o;
end

//Synchronizing ack signal from receiver
always@(posedge clk1_i)begin
    if(rst1_i)begin
        ack_r <= 0;
        synAck_r <= 0;
    end
    else {synAck_r, ack_r} <= {ack_r, ack_i};
end

//FSM sequential logic
always@(posedge clk1_i)begin
    if(rst1_i) curSt_r <= pStart;
    else      curSt_r <= nxtSt_r;
end

//FSM combinational logic
always@(*)begin
    req_o = 0;
    case(curSt_r)
        pStart: begin
            if(sendReady_i) begin
                req_o = 1;
                nxtSt_r = pWait;
            end
            else nxtSt_r = pStart;
        end
        pWait: begin
            if(synAck_r)begin
                req_o = 0;
                nxtSt_r = pStart;
            end
            else begin
                req_o = 1;
                nxtSt_r = pWait;
            end
        end
        default:begin

```

```

                                nxtSt_r = pStart;
                                end
                                endcase
                                end
endmodule

`define kDataW 8
`define kDataB `kDataW-1:0

module handShakeRec(
    clk2_i,
    rst2_i,
    dataIn_i,
    req_i,
    ack_o
);
    input          clk2_i;
    input          rst2_i;
    input[`kDataB] dataIn_i;
    input          req_i;
    output         ack_o;

    reg            ack_o;

    reg            req_r;
    reg            synReq_r;

    reg            load_r;

    reg[`kDataB]   data_r;

    reg[1:0]       curSt_r;
    reg[1:0]       nxtSt_r;

    parameter      pStart = 2'b00;
    parameter      pAck = 2'b01;
    parameter      pDone = 2'b10;

    //Receiving data from input
    always@(posedge clk2_i)begin
        if(rst2_i)          data_r <= 0;
        else if(load_r)      data_r <= dataIn_i;
        else                 data_r <= data_r;
    end

    //Synchronizing req signal from sender

```

```

always@(posedge clk2_i)begin
    if(rst2_i)begin
        req_r <= 0;
        synReq_r <= 0;
    end
    else {synReq_r, req_r} <= {req_r, req_i};
end

//FSM sequential logic
always@(posedge clk2_i)begin
    if(rst2_i) curSt_r <= pStart;
    else curSt_r <= nxtSt_r;
end
//FSM combinational logic
always@(*)begin
    ack_o = 0;
    load_r = 0;
    case(curSt_r)
    pStart: begin
        if(synReq_r) begin
            load_r = 1;
            ack_o = 1;
            nxtSt_r = pAck;
        end
        else nxtSt_r = pStart;
    end
    pAck: begin
        ack_o = 1;
        nxtSt_r = pDone;
    end
    pDone: begin
        ack_o = 0;
        nxtSt_r = pStart;
    end
    default:begin
        nxtSt_r = pStart;
    end
    endcase
end
endmodule

```

```

`include "handShakeSender.v"
`include "handShakeRec.v"

```

```

module handShakeTop(
    clk1_i,

```

```

        clk2_i,
        rst1_i,
        rst2_i,
        dataIn_i,
        sendReady_i
    );

    input          clk1_i;
    input          clk2_i;
    input          rst1_i;
    input          rst2_i;
    input[`kDataB] dataIn_i;
    input          sendReady_i;

    wire          ack_w;
    wire          req_w;
    wire[`kDataB] dataOut_w;

    handshakeSender uHandshakeSender(
        .clk1_i      (clk1_i),
        .rst1_i      (rst1_i),
        .dataIn_i     (dataIn_i),
        .sendReady_i (sendReady_i),
        .ack_i        (ack_w),
        .req_o         (req_w),
        .dataOut_o     (dataOut_w)
    );
    handshakeRec    uHandshakeRec(
        .clk2_i      (clk2_i),
        .rst2_i      (rst2_i),
        .dataIn_i     (dataOut_w),
        .req_i        (req_w),
        .ack_o         (ack_w)
    );

endmodule

```

3. FIFO

A. Sync. FIFO

1. Pointer Moving:

- a) $wrPt + 1$ ($wr_en \ \& \ !full$)
- b) $rdPt + 1$ ($rd_en \ \& \ !empty$)

2. Pointer Counter:

- a) Write Only ($!full \ \&\& \ wr_en$)

- ptCnt = ptCnt + 1
- b) Read Only (!empty && rd_en)
ptCnt = ptCnt - 1
- c) Write & Read Simultaneously ((!full && wr_en) && (!empty && rd_en))
ptCnt = ptCnt
- d) Don't write & read
ptCnt = ptCnt

3. One clock:

- a) Write data in (!full && wr_en)
b) Read data out (!empty && rd_en)

4. Full & Empty

- a) If ptCnt = 0, it is empty
b) If ptCnt = FIFO depth, it is full

```
`define kFIFOBitW      8
`define kFIFOBitS      `kFIFOBitW-1 : 0
`define kFIFOAdrW      4                // Bit of address
`define kFIFODepth      ( 1 << `kFIFOAdrW )    // Depth = 24
```

```
module syncFIFO(
```

```
    clk,
    rst,
    wrEn_i,
    rdEn_i,
    dIn_i,
    dOut_o,
    empty_o,
    full_o
```

```
);
```

```
    input                clk;
    input                rst;
    input                wrEn_i;
    input                rdEn_i;
    input[`kFIFOBitS]    dIn_i;
    output[`kFIFOBitS]    dOut_o;
    output                empty_o;
    output                full_o;
```

```
    reg[`kFIFOBitS]      dOut_o;
    reg[`kFIFOBitS]      FIFOMem[`kFIFODepth-1 : 0];
```

```
    reg[`kFIFOAdrW:0]    ptCnt;
    reg[`kFIFOAdrW-1:0]  wrPt;
    reg[`kFIFOAdrW-1:0]  rdPt;
```

```

//Pointer moving
always@(posedge clk)begin
    if(rst)begin
        wrPt <= 0;
        rdPt <= 0;
    end
    else if(!full_o && wrEn_i)    wrPt <= wrPt + 1;
    else if(!empty_o && rdEn_i) rdPt <= rdPt + 1;
end
//Pointer counter
always@(posedge clk)begin
    if(rst)    ptCnt <= 0;
    else if(!full_o && wrEn_i)    ptCnt <= ptCnt + 1;
    else if(!empty_o && rdEn_i) ptCnt <= ptCnt - 1;
    else if((!full_o && wrEn_i) && (!empty_o && rdEn_i))    ptCnt <= ptCnt;
    else    ptCnt <= ptCnt;
end
//Write data in
always@(posedge clk)begin
    if(!full_o && wrEn_i)    FIFOMem[wrPt] <= dIn_i;
end
//Read data out
always@(posedge clk)begin
    if(!empty_o && rdEn_i)    dOut_o <= FIFOMem[rdPt];
end
//Full & empty outputs
assign    full_o = (ptCnt == `kFIFODepth);
assign    empty_o = (ptCnt == 0);
endmodule

```

B. Async. FIFO

1. Port list: wClk, wRst, wrEn, wData, wFull / rClk, rRst, rdEn, rData, rEmpty
2. Pointer moving in binary:
 - a) wrPt + 1 (wr_en & !full)
 - b) rdPt + 1 (rd_en & !empty)
3. Pointer conversion from binary to Gray code


```

wrPt => grayWrPt
rdPr => grayRdPt

```
4. Pointer Synchronization:


```

grayWrPt => syncGrayWrPt
grayRdPt => syncGrayRdPt

```


5. Pointer from Gray code to binary

$\text{syncGrayWrPt} \Rightarrow \text{syncBinWrPt}$

$\text{syncGrayRdPt} \Rightarrow \text{syncBinRdPt}$

6. Full & Empty

a) Empty = 1

i. when $\text{syncBinWrPt} = \text{rdPt} + 1$ if (!empty && rdEn)

ii. when $\text{syncBinWrPt} = \text{rdPt}$ else


b) Full = 1

iii. when $\text{syncBinRdPt} = \text{wrPt} + 2$ if (!full && wrEn)

iv. when $\text{syncBinRdPt} = \text{wrPt} + 1$ else

7. Dual port memory(w/o read-clk) for wrPt / rdPt **not** syncWrPt / syncRdPt

8. Async. FIFO block diagram

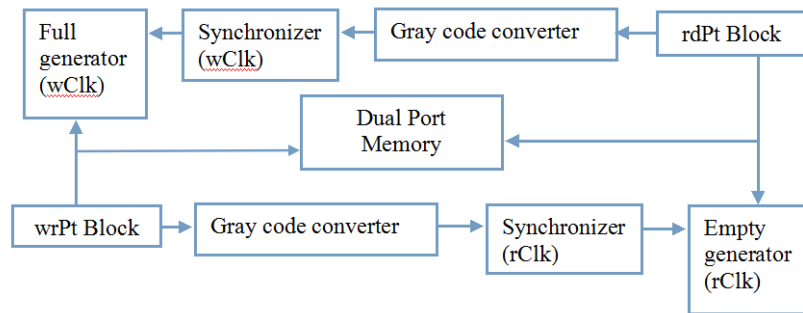

```
`define kFIFOBtW      8
`define kFIFOBtS      `kFIFOBtW-1 : 0
`define kFIFOAdrW      4                      // Bit of address
`define kFIFODepth     ( 1 << `kFIFOAdrW )    // Depth = 24
```

```
module asyncFIFO(
    wClk,
    wRst,
    wrEn_i,
    wData_i,
    wFull_o,

    rClk,
    rRst,
    rdEn_i,
    rData_o,
    rEmpty_o
);
```

```

input          wClk;
input          wRst;
input          wrEn_i;
input[`kFIFOBitS] wData_i;
output        wFull_o;
reg           wFull_o;

input          rClk;
input          rRst;
input          rdEn_i;
output[`kFIFOBitS] rData_o;
reg[`kFIFOBitS] rData_o;
output        rEmpty_o;
reg           rEmpty_o;

reg[`kFIFOAdrW-1:0] wrPt;
wire[`kFIFOAdrW-1:0] grayWrPt;
reg[`kFIFOAdrW-1:0] delayGrayWrPt;
reg[`kFIFOAdrW-1:0] syncGrayWrPt;
wire[`kFIFOAdrW-1:0] syncBinWrPt;

reg[`kFIFOAdrW-1:0] rdPt;
wire[`kFIFOAdrW-1:0] grayRdPt;
reg[`kFIFOAdrW-1:0] delayGrayRdPt;
reg[`kFIFOAdrW-1:0] syncGrayRdPt;
wire[`kFIFOAdrW-1:0] syncBinRdPt;

reg[`kFIFOBitS] FIFOMem[`kFIFODepth-1 : 0];

//Pointer moving in wClk/rClk
always@(posedge wClk)begin
    if(wRst) wrPt <= 0;
    else if(!wFull_o && wrEn_i) wrPt <= wrPt + 1;
end
always@(posedge rClk)begin
    if(wRst) rdPt <= 0;
    else if(!rEmpty_o && rdEn_i) rdPt <= rdPt - 1;
end

//Binary to Gray converter
function [`kFIFOBitS] bin2Gray;
    input[`kFIFOBitS] binDin;
    bin2Gray = binDin ^ (binDin>>1);
endfunction

assign grayWrPt = bin2Gray(wrPt);

```

```

assign      grayRdPt = bin2Gray(rdPt);

//Write/Read pointer synchronizer
always@(posedge wClk)begin
    if(wRst)begin
        delayGrayWrPt <= 0;
        syncGrayWrPt <=0;
    end
    else      {syncGrayWrPt, delayGrayWrPt}<={delayGrayWrPt, grayWrPt };
end
always@(posedge rClk)begin
    if(rRst)begin
        delayGrayRdPt <= 0;
        syncGrayRdPt <=0;
    end
    else      {syncGrayRdPt, delayGrayRdPt}<={delayGrayRdPt, grayRdPt };
end

//Gray to binary converter
function [`kFIFOBitS]    gray2Bin;
    input[`kFIFOBitS]    grayDin;
    integer               i;
    begin
        for(i = 0; i < `kFIFOBitW; i = i+1)
            gray2Bin[i] = ^(grayDin >> i);
    end
endfunction

assign      syncBinWrPt = gray2Bin(syncGrayWrPt );
assign      syncBinRdPt = gray2Bin(syncGrayRdPt );

//Full & empty outputs
always@(posedge rClk)begin
    if(rRst)      rEmpty_o <= 0;
    else if(!rEmpty_o && rdEn_i)      rEmpty_o <= (syncBinWrPt == rdPt + 1);
    else      rEmpty_o <= (syncBinWrPt == rdPt);
end
always@(posedge wClk)begin
    if(wRst)      wFull_o <= 0;
    else if(!wFull_o && wrEn_i)      wFull_o <= (syncBinRdPt == wrPt + 2);
    else      wFull_o <= (syncBinRdPt == wrPt + 1);
end

//Write-in/Read-out from memory
always@(posedge wClk)begin
    if(!wFull_o && wrEn_i)      FIFOMem[wrPt] <= wData_i;

```

```

end
always@(posedge rClk)begin
    if(!rEmpty_o && rdEn_i)    rData_o <= FIFOMem[rdPt];
end
endmodule

```

4. FIFO Depth Calculation

a) Equation:

WritingTime = number of data(needed for write-in) * $(1/f_{write})$

ReadingTime = number of data(same as above) * $(1/f_{read})$

TimeDifference = | WritingTime - ReadingTime |

Depth = TimeDifference * bigger(f_{write} , f_{read})

b) Examples:

i. f_{write} = 30MHz; f_{read} = 40MHz; 10 data should be transferred by FIFO

WritingTime = $10 * (1/30\text{MHz})$; ReadingTime = $10 * (1/40\text{MHz})$

Depth = $[10 * (1/30\text{MHz}) - 10 * (1/40\text{MHz})] * 40\text{MHz}$
 $= 3.333 \approx 4$

ii. f_{write} = 100MHz, 80data/100cycles

f_{read} = 80MHz, 80data/80cycles

Depth = $| [80 * (1/100\text{MHz}) - 80 * (1/80\text{MHz})] | * 100\text{MHz}$
 $= 20$

iii. Continuous write-in: 80 data/80 cycles


Burst write-in(20 data every time): 80 data/100 cycles, no data between two burst slots.

Read out continuously: 8data/10cycles

$f_{burstWrite} = f_{read} = 8 \text{ data/100 cycles}$

But $f_{continuous Write} > f_{read}$

 Considering worse case in 200 cycles, there are 160 data. But it may be 160 data in 160 cycles if continuously written in.



Depth = $160 * (80/80\text{cycles}) - 160 * (8/10\text{cycles}) = 32$