

EE461 Verilog-HDL

Week 4 UDP Design



Alex Yang, Engineering School, NPU



Week 4 outlines

- User Defined Primitives **(Non Synthesizable)**
 - Introduction
 - Syntax
 - UDP ports rules
 - Body
 - Symbols
 - Combinational UDPs
 - Level Sensitive Sequential UDP
 - Edge-Sensitive UDPs
 - UDP or Module Decision





Syntax

- UDP begins with reserve word `primitive` and ends with `endprimitive`.

```
primitive udpSyn (
```

```
        a_o,           // Port a  
        b_i,           // Port b  
        c_i,           // Port c  
        d-i           // Port d
```

```
);
```

```
        output a_0;  
        input  b_i,   c_i,   d_i;
```

```
        // UDP function code here
```

```
endprimitive
```



Introduction

- If built-in primitives in Verilog like gates, transmission gates and switches are not enough, Verilog provides UDP, or simply User Defined Primitives to generate more.
- The following models are included
 - Combinational Logic
 - Sequential Logic
- Timing information along with these UDPs could model complete ASIC library models.



UDP ports rules

- An UDP can contain only **one output** and up to 10 inputs.
- Output port should be the **first** port followed by one or more input ports.
- All UDP ports are **scalar**, i.e. Vector ports are not allowed.
- UDPs can **NOT** have bidirectional ports.
- The output terminal of a **sequential UDP** requires an additional declaration as type **reg**.
- It is illegal to declare a reg for the output terminal of a combinational UDP



UDP ports rules

- The state in a sequential UDP can be initialized with an 'initial' statement. This statement is optional. A 1-bit value is assigned to the output, which is declared as reg.
- The state table entries can contain values 0,1,or x .
UDPs do not handle z values. Z values passed to a UDP are treated x values.
- "inout" port can't be used in UDP.
- UDPs are defined at the same level as modules.
UDPs can not be defined inside modules. They can be instantiated only inside modules. UDPs are instantiated exactly like gate primitives.
- UDP primitive can't instantiate any other primitives or modules
- If more outputs are needed in UDP, instantiate more UPDs in top module
- **Nonsynthesizable**



- Functionality of Primitives: "table" and "endtable"

```
a_o,      // Port a
b_i,      // Port b
c_i       // Port c
```

```
output    a_o;
input     b_i,      c_i;
```

endprimitive



Body

```
`include "udpBody.v"
module udpBodyTB();
    reg  b_r, c_r;
    wire a_w;
    udpBody uUdpBody (
        a_w,
        b_r,
        c_r
    );
    initial begin
        $monitor(" B_i = %b C_i = %b A_o = %b", b_r, c_r, a_w);
        b_r = 0;
        c_r = 0;
        #1 b_r = 1;
        #1 b_r = 0;
        #1 c_r = 1;
        #1 b_r = 1'bx;
        #1 c_r = 0;
        #1 b_r = 1;
        #1 c_r = 1'bx;
        #1 b_r = 0;
        #1 $finish;
    end
endmodule
```

//This file and testbench must be under the same directory

Results:

```
B_i = 0 C_i = 0 A_o = 0
B_i = 1 C_i = 0 A_o = 1
B_i = 0 C_i = 0 A_o = 0
B_i = 0 C_i = 1 A_o = 1
B_i = x C_i = 1 A_o = 1
B_i = x C_i = 0 A_o = x
B_i = 1 C_i = 0 A_o = 1
B_i = 1 C_i = x A_o = 1
B_i = 0 C_i = x A_o = x
```




Body

■ Initial

- Initial statement is used for initialization of sequential logic UDPs.

primitive udpInit (

*a_o,
b_i,
c_i*

);

*output a_o;
input b_i, c_i;
reg a_o;*

initial a_o = 1'b1; // Variable in LHS must be "reg"
// Variables in RHS could be "reg" or "wire"

table
// udp_initial behaviour
endtable

endprimitive



Combinational UDPs

- Example:

primitive udpAnd (

out_o,
a_i, // Port list
b_i

);

output out_o; // Don't care order of port list in declaration

input a_i; // Output must be wire data type

input b_i;

table // a b : out; // Order of inputs must be the same as port list

0 0 : 0;

0 1 : 0;

1 0 : 0;

1 1 : 1;

// x x : x;

endtable

endprimitive

If all inputs are specified as x, then the output must be specified as x. All combinations that are not explicitly specified result in a default output state of x.



Combinational UDPs

■ State table entries

- `<input1><input2>.....<inputn>:<output>;`
The `<input#>` values must be in the same order as in the input list
- It is not necessary to explicitly specify every possible input combination. Output is `x` if the combinations are not explicitly.
- Create truth table first w/o considering `x` & `z`, and modify to shorthand format with “?”.
- It is **illegal** to have the same combination of inputs, specified for different outputs.

primitive udpAnd(f_o, a_i, b_i);

output f_o;

input a_i,

input b_i;

table

// a b : f;

1 1 : 1; // If adding one more line, like a = 1 and b = 1, f=0, it is illegal.

0 ? : 0;

? 0 : 0; // ? expanded to 0, 1, x

endtable

endprimitive



Combinational UDPs

■ Instantiation of UDPs

```
`include "udpXOR.v"
```

```
`include "udpAND.v"
```

```
`include "udpOR.v"
```

```
module udpFA(sum, cout, x, y, cin);
```

```
    output sum, cout;
```

```
    input x, y, cin;
```

```
    wire s1, c1, c2;
```

```
    // instantiate udp primitives
```

```
    udpXOR    (s1, x, y);
```

```
    udpAND    (c1, x, y);
```

```
    udpXOR    (sum, s1, cin);
```

```
    udpAND    (c2, s1, cin);
```

```
    udpOR     (cout, c1, c2);
```

```
endmodule
```

//Unit name is optional





Level Sensitive Sequential UDP

■ State table entries

<input1><input2>.....<inputn>:<current_state>:<next_state>;

- The output is always declared as a reg
- An initial statement can be used to initialize output

primitive dLatch(q, d, gate, clear);

output q;

input d, gate, clear;

reg q;

initial q = 0;

// initialize output q

table

// d gate clear : q : q+;

? ? 1 : ? : 0 ;

// clear

1 1 0 : ? : 1 ;

// latch q = 1

0 1 0 : ? : 0 ;

// latch q = 0

? 0 0 : ? : - ;

// no change

endtable

endprimitive



Edge-Sensitive UDPs

- State table entries

- All unspecified transitions default to the output value x
- All transitions that should not affect the output must be explicitly specified. Otherwise, they will cause the value of the output to change to x .
- If the UDP is sensitive to edges of any input, the desired output state must be specified for all edges of all inputs.





Edge-Sensitive UDPs

- State table entries

- It is important to completely specify the UDP by covering all possible combinations of edge transitions and levels in the state table for which the outputs have a known value. Otherwise, some combinations may result in an unknown value.

- Only one edge specification is allowed per table entry. More than one edge specification in a single table entry is illegal in Verilog.







Symbols

Symbol	Interpretation	Explanation
?	0 or 1 or X	? means the variable can be 0 or 1 or x
b	0 or 1	Same as ?, but x is not included
f	(10)	Falling edge on an input
r	(01)	Rising edge on an input
p	(01) or (0x) or (x1) or (1z) or (z1)	Rising edge including x and z
n	(10) or (1x) or (x0) or (0z) or (z0)	Falling edge including x and z
*	(??)	All transitions
-	no change	No Change



Edge-Sensitive UDPs

■ D Flip Flop & T Flip Flop

  

D	Q	Q ⁺	Operation
0	0	0	Reset
0	1	0	Reset
1	0	1	Set
1	1	1	Set

T	Q	Q ⁺	Operation
0	0	0	Hold
0	1	1	Hold
1	0	1	Toggle
1	1	0	Toggle



Edge-Sensitive UDPs

- Example:

```
primitive TFF(q, clk, clear);
    output q;
    input  clk,    clear;
    reg    q;
    // define the behavior of edge-triggered T_FF
    table
        // clk clear : q : q+;
        ?      1 : ? : 0 ;           // asynchronous clear
        ?  (10) : ? : - ;           // ignore negative edge of clear
        (01)   0 : 1 : 0 ;           // toggle at positive edge
        (01)   0 : 0 : 1 ;           // of clk
        (1?)   0 : ? : - ;           // ignore negative edge of clk
    endtable
endprimitive
```



Edge-Sensitive UDPs

▪ Example:

```
primitive DFF(q, d, clk, reset);
```

```
    output q;
```

```
    input d, clk, reset;
```

```
    reg q;
```

```
    table
```

```
        // d  clk reset : q : q+;
```

```
        ?  ?      1 : ? : 0 ;
```

```
        ?  ?  (10) : ? : - ;
```

```
// output = 1, if clear = 1
```

```
// ignore negative edge of clear
```

```
        1 (10)   0 : ? : 1 ;
```

```
// Get data at falling edge of
```

```
        0 (10)   0 : ? : 0 ;
```

```
// clock
```

```
        ? (1x)   0 : ? : - ;
```

```
// Hold q if clock goes to x state
```



Edge-Sensitive UDPs

- Example:

```
// d  clk reset : q : q+;  
? (0?)  0 : ? : - ;      //Ignore negative edge of clear  
? (x1)  0 : ? : - ;      // Ignore negative edge of clear  
  
  (??)  ?    0 : ? : - ;   //Ignore any changes of d w/o  
                                // clock edge trigger  
  
    endtable  
endprimitive
```

Notice that the following statement is illegal

table

... ..

(01) (10) 0: ? : -;

... ..

endtable

// Illegal; 2 transitions in one entry





Edge-Sensitive UDPs

■ Instantiation of UDPs

```
`include "TFF.v"
```

```
module rippleCounter(clock, clear, q);
```

```
    input          clock;
```

```
    input          clear;
```

```
    output [3:0] q;
```

```
// instantiate the T_FF.s.
```

```
    TFF  uTFF0
```

```
        (q[0], clock, clear);
```

```
    TFF  uTFF1
```

```
        (q[1], q[0], clear);
```


```
    TFF  uTFF2
```

```
        (q[2], q[1], clear);
```

```
    TFF  uTFF3
```

```
        (q[3], q[2], clear);
```

```
endmodule
```

 

UDP or Module Decision

- UDPs model functionality only without timing or process technology information(such as CMOS, TTL, ECL). The primary purpose of a UDP is to define the functional portion of a block in a simple and concise form.
- UDP is only for one output terminal. For more than one output, module should be used.
- Verilog simulators are required to allow a max of 9 inputs for sequential UDPs and 10 for combinational UDPs.
- It is not advisable to design a block with a large number of inputs as a UDP due to large memory spaces demanded
- UDPs are not always the appropriate method to design a block. Sometimes it is easier to design blocks as a module, such as an 8-to-1 multiplexer design. RTL level design would be much simpler, instead of UDP with large number of table entries. Indeed, It is important to consider complexity trade-offs for UDP selection