

Data Communication Module Designs

Alex Yang
Engineering School, NPU

UART Design


- Introduction to UART
- Transmitter Design
- Receiver Design
- Clock Generator
- Top Level Design

I. Introduction:

UART: Universal asynchronous receiver/transmitter. UARTs are commonly used in conjunction with communication standards such as EIA_RS-232, RS-422 or RS-485. Bit0-bit7 are ASCII code and “Parity” is for error check. UART will add “start” and “stop” bits for communication with outside device.

Stop Bit	Parity Bit	Data Bit 6	Data Bit 5	Data Bit 4	Data Bit 3	Data Bit 2	Data Bit 1	Data Bit 0	Start Bit
----------	------------	------------	------------	------------	------------	------------	------------	------------	-----------

UART Architecture:

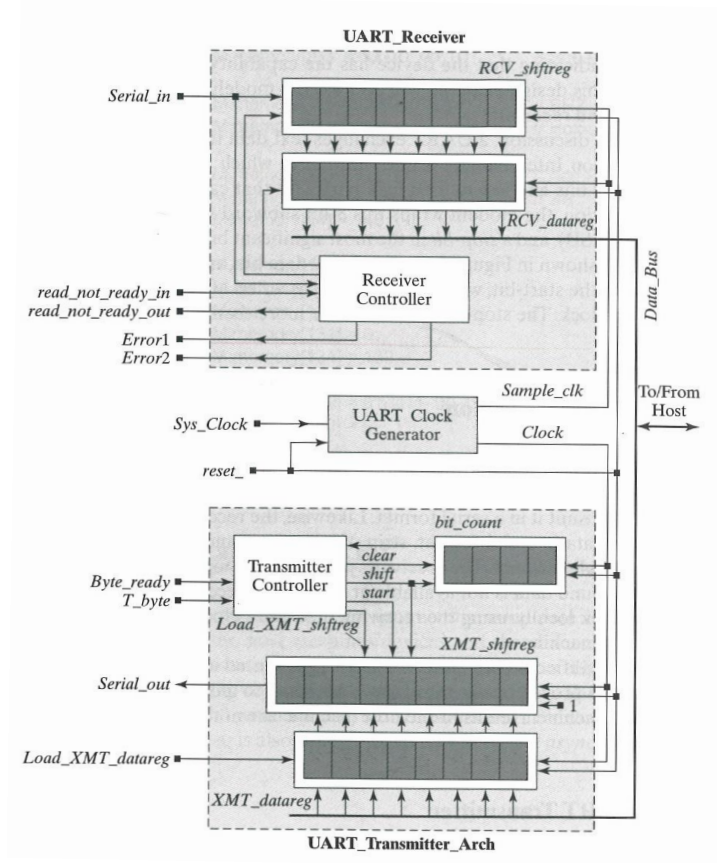

II. UART Transmitter Design

- UART Transmitter Signals:


- Input signals:

- 1) **Byte_ready** from host computer is to indicate that the data in the bus is valid
- 2) **Load_XMT_datareg** from host computer is to tell UART to load data in the bus
- 3) **T_byte** from host computer is to ask UART to send data out.
- 4) **Data** in the Bus
- 5) **Reset** in UART
- 6) **Clock** in UART

- Output signals:

- 1) **SeriesOut**

- FSM's Algorithm diagram in Transmitter

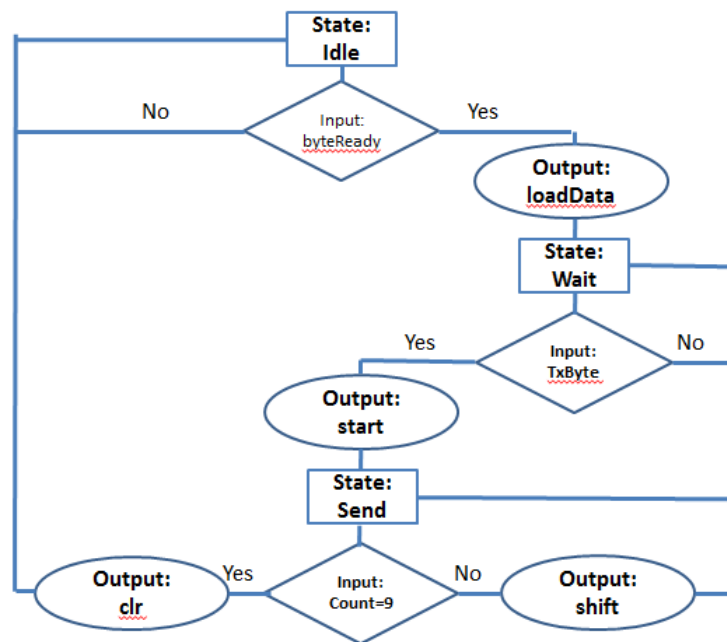

- Transmitter Verilog Code:

```
module UARTTx(
    clk,
    rst_i,
    byteReady_i,
    load_i,
    TxByte_i,
    busData_i,
    serialOut_o
);
input  clk;
input  rst_i;
input  byteReady_i;
```

```

input  load_i;
input  TxByte_i;
input[7:0] busData_i;
output serialOut_o;

parameter pIdle=2'b00;
parameter pWait=2'b01;
parameter pSend=2'b10;

reg[1:0]  curSt_r;
reg[1:0]  nxtSt_r;

reg  loadData_r;
reg  start_r;
reg  clr_r;
reg  shift_r;
reg[3:0] cnt_r;

reg[7:0] busReg_r;
reg[8:0] dataReg_r;

//Sequential Logic
always@(posedge clk)begin
    if(rst_i)begin
        curSt_r <= pIdle;
    end
    else begin
        curSt_r <= nxtSt_r ;
    end
end
// Combo Logic
always@(*)begin
    loadData_r=1'b0;
    start_r=1'b0;
    clr_r=1'b0;
    shift_r=1'b0;
    case(curSt_r)
        pIdle: begin
            if(byteReady_i)begin
                loadData_r=1'b1;
                nxtSt_r=pWait;
            end
            else nxtSt_r=pIdle;
        end
        pWait: begin
            if(TxByte_i)begin
                start_r = 1'b1;
                nxtSt_r= pSend;
            end
            else nxtSt_r=pWait;
        end
        pSend: begin
            if(cnt_r ==9)begin
                clr_r = 1'b1;

```

```


        nxtSt_r= pIdle;
    end
    else begin
        shift_r = 1'b1;
        nxtSt_r=pSend;
    end
end
default: begin
    nxtSt_r= 2'bxx;
end
endcase
end
//Implementation block- bit counter
always@(posedge clk)begin
    if(rst_i)begin
        cnt_r<=4'b0000;
    end
    else if(clr_r)begin
        cnt_r<=4'b0000;
    end
    else if(shift_r)begin
        cnt_r<= cnt_r + 1'b1;
    end
end

always@(posedge clk)begin
    if(rst_i)begin
        busReg_r <=8'b0000_0000;
        dataReg_r<=9'b1_1111_1111;
    end
    else if(load_i)begin
        busReg_r <= busData_i;
    end
    else if(loadData_r)begin
        dataReg_r <= {busReg_r, 1'b1 };
    end
    else if(start_r)begin
        dataReg_r[0]<=1'b0; //output startbit ==0;
    end
    else if(shift_r)begin
        dataReg_r<={ 1'b1, dataReg_r[8:1] };
    end
end
    assign serialOut_o = dataReg_r[0];
endmodule

```


- Verification waveforms:

 Simulation: busData_i = 8'b1010_1010
 serialOut_o = 0 1 0 1 0 1 0 1



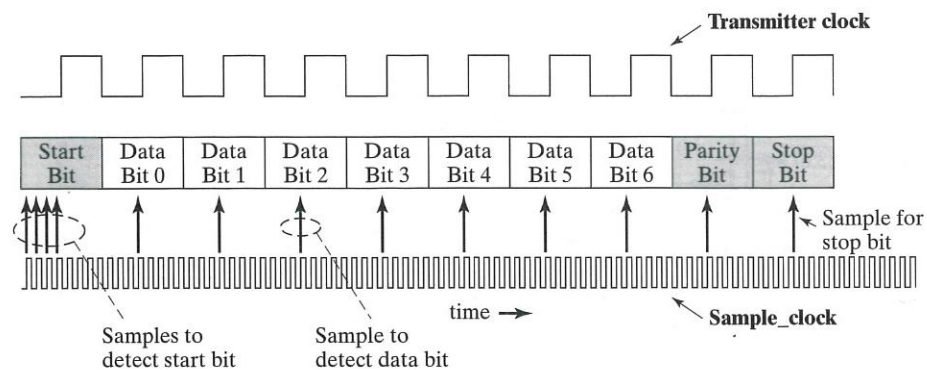
III. UART Receiver Design

Data received by UART don't include clock signal. UART will use higher frequency clock to sample each bit for input data. Usually, sampling frequency in receiver is 8 times frequency of input data.



- Input signals
 - 1) **notReady** from host computer is to indicate that host is not ready to receive.
 - 2) **serialIn** from outside device
 - 3) **sampleClk** is 8 times frequency of transmitter clk
 - 4) **rst**
- Output signals
 - 1) **dataOut** is to send to host computer
 - 2) **askReady** is to ask if host computer is ready to receive or not
 - 3) **err1** is to indicate the host is not ready to receive
 - 4) **err2** is to send to outside device to indicate the missing stop bit

- FSM's algorithm diagram

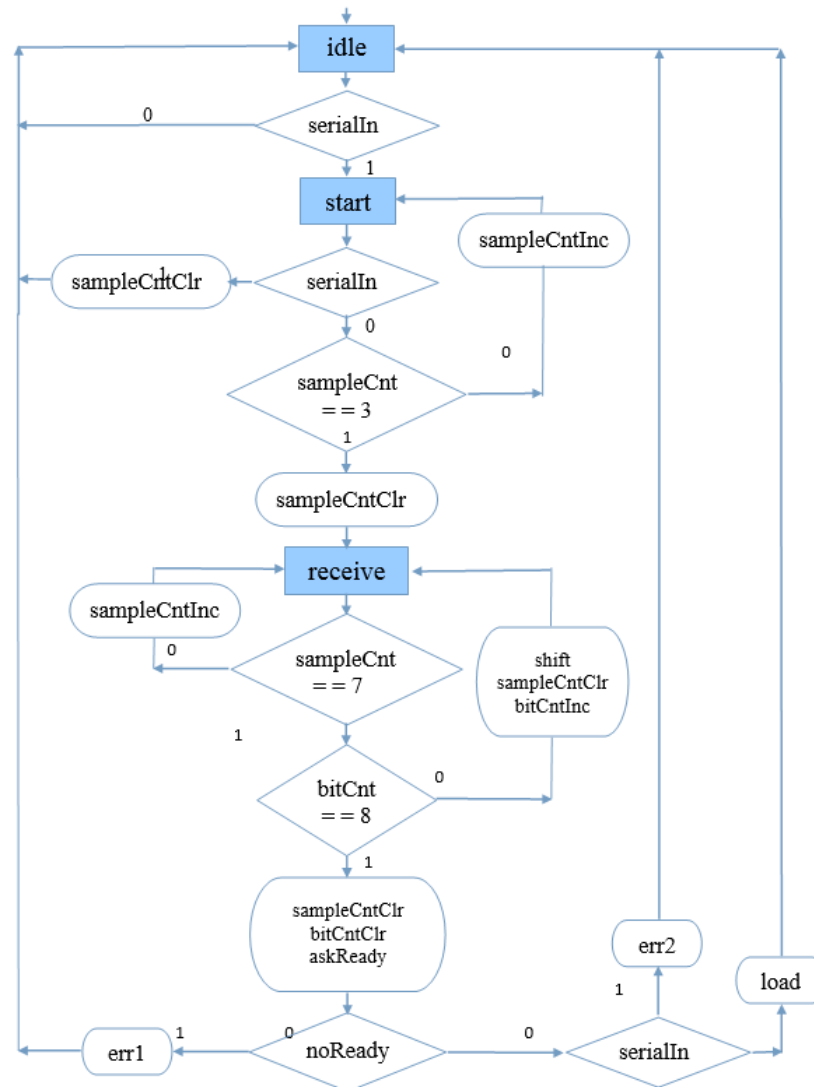

- Receiver Verilog Code

```

module UARTRx(
    rst_i,
    sampleClk,
    serialIn_i,
    noReady_i,
    dataOut_o,
    askReady_o,
    err1_o,
    err2_o
);
    input rst_i;
    input sampleClk;
    input serialIn_i;
    input noReady_i;
    output[7:0] dataOut_o;
    output askReady_o;
  
```

```

output      err1_o;
output      err2_o;

reg         askReady_o;

parameter   pIdle=2'b00;
parameter   pStart=2'b01;
parameter   pRec=2'b10;

```

```

reg[1:0]     curSt_r;
reg[1:0]     nxtSt_r;

reg[2:0]     sampleCnt_r;
reg          sampleCntClr_r;
reg          sampleCntInc_r;
reg[3:0]     bitCnt_r;
reg          bitCntInc_r;
reg          bitCntClr_r;
reg          err1_o;
reg          err2_o;
reg          load_r;
reg          shift_r;
reg[7:0]     shiftReg;
reg[7:0]     dataOut_o;

```

```

//FSM-Sequential logic block
always@(posedge sampleClk)begin
    if(rst_i)begin
        curSt_r<=pIdle;
    end
    else begin
        curSt_r<=nxtSt_r;
    end
end

```

```

//FSM-Combinational logic block

```

```

always@(*)begin
    sampleCntClr_r=1'b0;
    shift_r=1'b0;
    sampleCntInc_r=1'b0;
    bitCntInc_r=1'b0;
    bitCntClr_r=1'b0;
    askReady_o=1'b0;
    err1_o=1'b0;
    load_r=1'b0;
    err2_o=1'b0;
    nxtSt_r=curSt_r;

    case(curSt_r)
        pIdle:begin
            if(serialIn_i==0)begin
                nxtSt_r=pStart;
            end

```

```

        else nxtSt_r=pIdle;
    end
    pStart: begin
        if(serialIn_i!=0)begin
            sampleCntClr_r=1'b1;
            nxtSt_r=pIdle;
        end
        else if(sampleCnt_r==3'b011)begin
            sampleCntClr_r=1'b1;
            nxtSt_r=pRec;
        end
        else begin
            sampleCntInc_r=1'b1;
            nxtSt_r=pStart;
        end
    end
end
pRec:begin
    if(sampleCnt_r==3'b111)begin
        if(bitCnt_r!=4'b1000)begin
            shift_r=1'b1;
            sampleCntClr_r=1'b1;
            bitCntInc_r=1'b1;
            nxtSt_r=pRec;
        end
        else begin
            sampleCntClr_r=1'b1;
            bitCntClr_r=1'b1;
            askReady_o=1'b1;
            if(noReady_i==1'b1)begin
                err1_o=1'b1;
                nxtSt_r=pIdle;
            end
            else begin
                if(serialIn_i!=0)begin
                    load_r=1'b1;
                    nxtSt_r=pIdle;
                end
                else begin
                    err2_o=1'b1;
                    nxtSt_r=pIdle;
                end
            end
        end
    end
end
end
else begin
    sampleCntInc_r=1'b1;
    nxtSt_r=pRec;
end
end

end
default:begin
    nxtSt_r=2'bxx;
end
endcase

```



```


end

//Implementation
always@(posedge sampleClk)begin
    if(rst_i)begin
        sampleCnt_r<=3'b000;
    end
    else if(sampleCntClr_r)begin
        sampleCnt_r<=3'b000;
    end
    else if(sampleCntInc_r)begin
        sampleCnt_r<=sampleCnt_r+1'b1;
    end
    // else begin
    //     sampleCnt_r<=sampleCnt_r;    //Redundant code
    // end
end
always@(posedge sampleClk)begin
    if(rst_i)begin
        bitCnt_r<=4'b0000;
    end
    else if(bitCntClr_r)begin
        bitCnt_r<=4'b0000;
    end
    else if(bitCntInc_r)begin
        bitCnt_r<=bitCnt_r+1'b1;
    end
    // else begin
    //     bitCnt_r<=bitCnt_r;          //Redundant code
    // end
end
always@(posedge sampleClk)begin
    if(rst_i)begin
        shiftReg<=8'b0000_0000;
        dataOut_o<=8'b0000_0000;
    end
    else if(shift_r)begin
        shiftReg[7:0]={ serialIn_i,shiftReg[7:1]};
    end
    else if(load_r)begin
        dataOut_o[7:0]<=shiftReg[7:0];
    end
end
end
endmodule

```


- Verification waveforms:

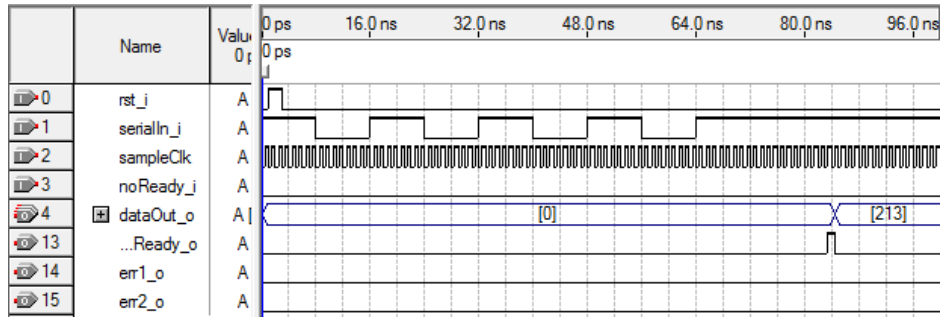Simulation: serialIn_i = 0(start) 1 0 1 0 _1 0 1 1(parity) 1 (stop)
 dataOut_o = 8'b1101_0101 (Decimal # : 213)



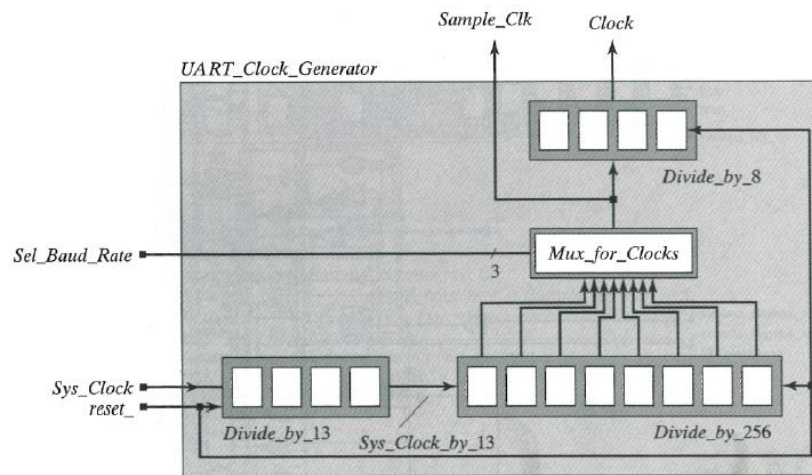IV. Clock Generator

In UART architecture diagram, there is clock generator block to output two clock signals sampleClk and Clk with the different frequencies, namely that sampleClk is 8 times of Clk. Assuming systemClk is 8MHz, design this block based on baud rate in the following table.



brSel	sampleClk	cslk
000	307,696	38462
001	153,838	19231
010	76,920	9615
011	38,464	4808
100	18,232	2404

101	9,616	1202
110	4,808	601
111	2,404	300.5

```

module Div13(
    sysClk,
    rst_i,
    sysClkDiv13_o
);
    input  sysClk;
    input  rst_i;
    output sysClkDiv13_o;

    reg[3:0] cnt_r;

    assign sysClkDiv13_o = cnt_r[3];

    // wire Clk1 = (cnt_r == 12);
    // wire Clk2 = (cnt_r > 6);

    always@(posedge sysClk)begin
        if(rst_i)begin
            cnt_r <=4'b0000;
        end
        else if(cnt_r == 4'd12)begin
            cnt_r <=4'd0;
        end
        else begin
            cnt_r <= cnt_r + 1;
        end
    end
endmodule

`include "Div13.v"
module clkGen(
    sysClk,
    rst_i,
    brSel,          //Baud Rate select

    sampleClk_o,
    clk_o
);
    input  sysClk;
    input  rst_i;
    input  brSel;    //Baud Rate select

    output sampleClk_o;
    output clk_o;

```

```

wire          sysClkDiv13_w;
reg[7:0]      Div256_r;
reg[2:0]      Div8_r;

Div13         uDiv13(
                .sysClk          (sysClk),
                .rst_i           (rst_i),
                .sysClkDiv13_o   (sysClkDiv13_w)
            );

always@(posedge sysClkDiv13_w)begin
    if(rst_i)      Div256_r <= 0;
    else          Div256_r <= Div256_r + 1;
end
always@(*)begin
    case(brSel)
        3'b000:    sampleClk_o = Div256_r[0];
        3'b001:    sampleClk_o = Div256_r[1];
        3'b010:    sampleClk_o = Div256_r[2];
        3'b011:    sampleClk_o = Div256_r[3];
        3'b100:    sampleClk_o = Div256_r[4];
        3'b101:    sampleClk_o = Div256_r[5];
        3'b110:    sampleClk_o = Div256_r[6];
        3'b111:    sampleClk_o = Div256_r[7];
        default:    sampleClk_o = 0;
    endcase
end
always@(posedge sampleClk_o)begin
    if(rst_i)      Div8_r <= 0;
    else          Div8_r <= Div8_r + 1;
end
assign          clk_o = Div8_r[2];
endmodule

```

V. Top Level Design

```

`include      "UARTTx.v"
`include      "UARTRx.v"

module Top(
    TxClk,          // From other block in the same chip
    rst_i,          // From other block in the same chip
    TxByteReady_i,  // From other block in the same chip
    TxLoad_i,       // From other block in the same chip
    TxByte_i,       // From other block in the same chip
    TxData_i,       // From other block in the same chip
    TxDout_o,       // To outside of the chip

    RxClk,          // From other block in the same chip
    RxDin_i,        // From outside of the chip
    RxNoReady_i,    // From other block in the same chip
    RxDout_o,       // To other block in the same chip
    RxAskReady_o,   // To other block in the same chip

```

```

        RxErr1_o,          // To other block in the same chip
        RxErr2_o          // To other block in the same chip
    );

    input          Txclk;
    input          rst_i;
    input          TxByteReady_i;
    input          TxLoad_i;
    input          TxByte_i;
    input          TxData_i;
    output[7:0]    TxDout_o;

    input          RxClk;
    input          RxDin_i;
    input          RxNoReady_i;
    output[7:0]    RxDout_o;
    output         RxAskReady_o;
    output         RxErr1_o;
    output         RxErr2_o;

    UARTTx        uUARTTx(
        .clk        (Txclk),
        .rst_i      (rst_i),
        .byteReady_i (TxByteReady_i),
        .load_i     (TxLoad_i),
        .TxByte_i   (TxByte_i),
        .busData_i  (TxData_i),
        .serialOut_o (TxDout_o)
    );
    UARTRx        uUARTRx(
        .rst_i      (rst_i),
        .sampleClk  (RxClk),
        .serialIn_i  (RxDin_i),
        .noReady_i   (RxNoReady_i),
        .dataOut_o   (RxDout_o),
        .askReady_o  (RxAskReady_o),
        .err1_o      (RxErr1_o),
        .err2_o      (RxErr2_o)
    );
endmodule

```